

COMBINATIONAL LOGIC

Satish Chandra
 Assistant Professor
 Department of Physics
 P P N College, Kanpur
www.satish0402.weebly.com

LOGIC GATES

- A circuit with an output signal that is logical function of the inputs.
- A circuit with one or more input voltages but only one output voltage.
- They are of two types
 1. Basic gates – NOT, OR & AND.
 2. Combinational gates
 - a) Universal gates – NOR & NAND
 - b) Arithmetic gates – Ex-OR & Ex-NOR.

CE NPN Transistor Circuit

Equivalent CE Circuit

Transistor as a switch

Logic Circuits

BASIC GATES

Transistor Inverter

V _{in}	V _{out}
LOW	HIGH
HIGH	LOW

NOT Gate

$V_{in} \rightarrow \text{NOT} \rightarrow V_{out}$
 $A \rightarrow \text{NOT} \rightarrow Y$
 $Y = \bar{A}$

A	Y
0	1
1	0

NOT Gate

- A gate with only one input and one output.
- Output state is always opposite the input state
- An INVERTER.

OR Gates

CASE 1: A is low and B is low.
CASE 2: A is low and B is high.
CASE 3: A is high and B is low.
CASE 4: A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 10

Two-input OR gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$Y = A + B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 11

Three-input OR gate

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$Y = A + B + C$

9:18:18 PM Satish Chandra, P P N College, Kanpur 12

OR Gate Symbols

Two-input $Y = A + B$

Three-input $Y = A + B + C$

Four-input $Y = A + B + C + D$

9:18:18 PM Satish Chandra, P P N College, Kanpur 13

OR Gate

- Two or more input signals but only one output signal.
- Output is high if **any** or **all** of the inputs are high.
- Logical Symbol
- OR gate performs logical addition
- Boolean expression $Y = A + B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 14

OR Gate

CASE 1: A is low and B is low.
CASE 2: A is low and B is high.
CASE 3: A is high and B is low.
CASE 4: A is high and B is high

9:18:18 PM Satish Chandra, P P N College, Kanpur 15

AND Gates

CASE 1: A is low and B is low.
CASE 2: A is low and B is high.
CASE 3: A is high and B is low.
CASE 4: A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 16

Two-input AND Gate

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$Y = A.B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 17


Three-input AND Gate


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


$Y = A.B.C$

9:18:18 PM Satish Chandra, P P N College, Kanpur 18

AND Gate Symbols

Two-input  $Y = A.B$


Three-input  $Y = A.B.C$

Four-input  $Y = A.B.C.D$

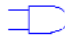9:18:18 PM Satish Chandra, P P N College, Kanpur 19


AND Gate

- Two or more input signals but only one output signal.
- Output is high if **all** of the inputs are high.
- Logical Symbol
- AND gate performs logical multiplication
- Boolean expression $Y = A.B$



9:18:18 PM Satish Chandra, P P N College, Kanpur 20

AND Gate

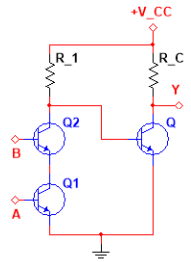

CASE 1:
A is low and B is low.

CASE 2:
A is low and B is high.

CASE 3:
A is high and B is low.

CASE 4:
A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 21

Logic Circuits

BOOLEAN ALGEBRA

9:18:18 PM Satish Chandra, P P N College, Kanpur 22

Boolean Algebra

- OR Addition Laws**
 - $A + 0 = A$
 - $A + 1 = 1$
 - $A + A = A$
 - $A + \bar{A} = 1$
- AND Multiplication Laws**
 - $A.0 = 0$
 - $A.1 = A$
 - $A.A = A$
 - $A.\bar{A} = 0$

9:18:18 PM Satish Chandra, P P N College, Kanpur 23

Boolean Algebra

- Commutative Laws**
 - $A + B = B + A$
 - $A.B = B.A$
- Associative Laws**
 - $A + (B + C) = (A + B) + C$
 - $A.(B.C) = (A.B).C$

9:18:18 PM Satish Chandra, P P N College, Kanpur 24

Boolean Algebra

- Distributive Laws**
 - $A(B + C) = A.B + A.C$
 - $A + B.C = (A + B).(A + C)$
- Absorptive Laws**
 - $A + A.B = A$
 - $A.(A + B) = A$
 - $A.(\bar{A} + B) = AB$
 - $A + \bar{A}.B = A + B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 25

Boolean Algebra

- Complement Theorem**
 - $\bar{\bar{A}} = A$
- De Morgan's Theorem**
 - $\overline{A + B} = \bar{A}.\bar{B}$
 - $\overline{A.B} = \bar{A} + \bar{B}$

9:18:18 PM Satish Chandra, P P N College, Kanpur 26

Logic Circuits

UNIVERSAL GATES & ARITHMETIC GATES

9:18:18 PM Satish Chandra, P P N College, Kanpur 27

NOR Gate

CASE 1:
A is low and B is low.

CASE 2:
A is low and B is high.

CASE 3:
A is high and B is low.

CASE 4:
A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 28

NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$Y = \overline{A+B}$

9:18:18 PM Satish Chandra, P P N College, Kanpur 29

NOR Gate

- Two or more input signals but only one output signal.
- Output is low if **any or all** of the inputs are high.
- Logical Symbol
- Boolean expression

$Y = \overline{A+B}$

9:18:18 PM Satish Chandra, P P N College, Kanpur 30

NOR Gate

CASE 1:
A is low and B is low.

CASE 2:
A is low and B is high.

CASE 3:
A is high and B is low.

CASE 4:
A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 31

NOR as a Universal gate

- NOT Gate
- OR Gate
- AND Gate

9:18:18 PM Satish Chandra, P P N College, Kanpur 32

NAND Gate

CASE 1:
A is low and B is low.

CASE 2:
A is low and B is high.

CASE 3:
A is high and B is low.

CASE 4:
A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 33

NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

$Y = \overline{AB}$

9:18:18 PM Satish Chandra, P P N College, Kanpur 34

NAND Gate

CASE 1:
A is low and B is low.

CASE 2:
A is low and B is high.

CASE 3:
A is high and B is low.

CASE 4:
A is high and B is high.

9:18:18 PM Satish Chandra, P P N College, Kanpur 35

NAND as a Universal gate

- NOT Gate
- OR Gate
- AND Gate

9:18:18 PM Satish Chandra, P P N College, Kanpur 36

Ex-OR Gate

$Y = \bar{A}B + A\bar{B}$

9:18:18 PM Satish Chandra, P P N College, Kanpur 37

Ex-OR Gate

$Y = \bar{A}B + A\bar{B}$
 $Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

9:18:18 PM Satish Chandra, P P N College, Kanpur 38

Ex-OR Gate

- Two or more input signals but only one output signal.
- Output is high if the inputs are **different**.
- Logical Symbol
- Boolean expression $Y = A \oplus B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 39

Ex-NOR Gate

$Y = \overline{\bar{A}B + A\bar{B}}$

$Y = A \oplus B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 40

Ex-NOR Gate

$Y = \overline{\bar{A}B + A\bar{B}}$
 $Y = A \oplus B$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

9:18:18 PM Satish Chandra, P P N College, Kanpur 41

Ex-NOR Gate

- Two or more input signals but only one output signal.
- Output is high if the inputs are **same**.
- Logical Symbol
- Boolean expression $Y = A \oplus B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 42

APPLICATIONS – PARITY CHECKER

$Y = 0$ for even parity
 $Y = 1$ for odd parity

9:18:18 PM Satish Chandra, P P N College, Kanpur 43

APPLICATIONS – BINARY TO GRAY CODE CONVERTER

BINARY → 1 0 0 1 1 0
 GRAY → 1 1 0 1 0 0

9:18:18 PM Satish Chandra, P P N College, Kanpur 44

Logic Circuits


ARITHMETIC CIRCUITS

9:18:18 PM Satish Chandra, P P N College, Kanpur 45

HALF ADDER

- An elementary circuit.
- Used to add two binary digits at a time.
- It performs binary addition
- Consists of an **XOR gate** whose output gives the **sum** and an **AND gate** whose output gives the **carry** of addition.


HALF ADDER

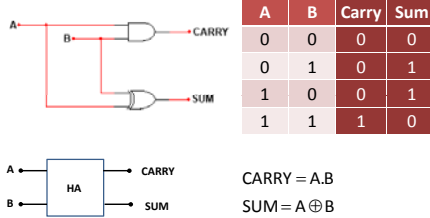


FULL ADDER

- Used to add **three binary digits** at a time.
- It performs binary addition of two bits and a carry.
- Consists of two half adders and an OR gate.

FULL ADDER

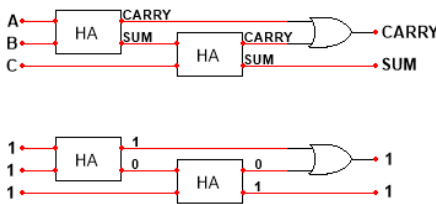


FULL ADDER

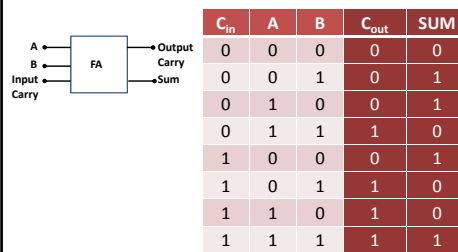


PARALLEL BINARY ADDER

- Used to add two binary numbers. For example
- $$\begin{array}{r} A_3 A_2 A_1 A_0 \\ B_3 B_2 B_1 B_0 \\ \hline S_4 S_3 S_2 S_1 S_0 \end{array}$$
- First column needs only a Half Adder. For any other column (except First), use Full Adder.

4 BIT PARALLEL BINARY ADDER

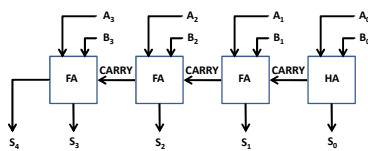

4 BIT PARALLEL BINARY ADDER

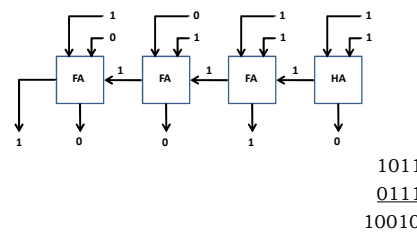

HALF SUBTRACTOR

- An elementary circuit used to subtract one binary digit from another.
- It performs binary subtraction handles two bits at a time and can be used for the LSB column.
- Consists of an **XOR gate** whose output gives the **difference** and an **AND gate** whose output gives the **borrow** of subtraction.
- One input of AND gate inverts itself using the **NOT gate**.

HALF SUBTRACTOR

A	B	Borrow	Difference
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

$BORROW = \bar{A} \cdot B$
 $DIFFERENCE = A \oplus B$

9:18:18 PM Satish Chandra, P P N College, Kanpur 55

FULL SUBTRACTOR

- Used to subtract **two binary digits** with **one borrow digit** at a time.
- It performs binary subtraction of two bits and a borrow and can be used for higher order columns.
- Consists of two half subtractors and an OR gate.

9:18:18 PM Satish Chandra, P P N College, Kanpur 56

FULL SUBTRACTOR

9:18:18 PM Satish Chandra, P P N College, Kanpur 57

FULL SUBTRACTOR

Bo _{in}	A	B	Bo _{out}	Differ
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

9:18:18 PM Satish Chandra, P P N College, Kanpur 58

PARALLEL BINARY SUBTRACTOR

- Used to subtract two binary numbers. For example

$$\begin{array}{r} A_3 A_2 A_1 A_0 \\ - B_3 B_2 B_1 B_0 \\ \hline S_3 S_2 S_1 S_0 \end{array}$$

- First column needs only a Half Subtractor. For any other column (except First), use Full Subtractor.

9:18:18 PM Satish Chandra, P P N College, Kanpur 59

4 BIT PARALLEL BINARY SUBTRACTOR

9:18:18 PM Satish Chandra, P P N College, Kanpur 60

4 BIT PARALLEL BINARY SUBTRACTOR

$$\begin{array}{r} 1001 \\ - 0110 \\ \hline 0011 \end{array}$$

9:18:18 PM Satish Chandra, P P N College, Kanpur 61

Logic Circuits








DATA PROCESSING CIRCUITS

9:18:18 PM Satish Chandra, P P N College, Kanpur 62

MULTIPLEXERS

- Multiplex means **many into one**.
- A circuit with **many inputs** but only **one output**.
- By applying **control signals**, only one selected input can be transmitted to the output.
- Also called a **data selector**, because the output bit depends on the input data bit that is selected.

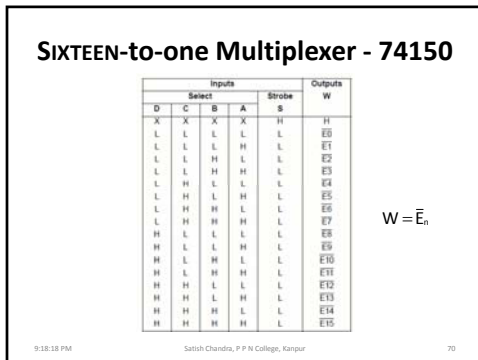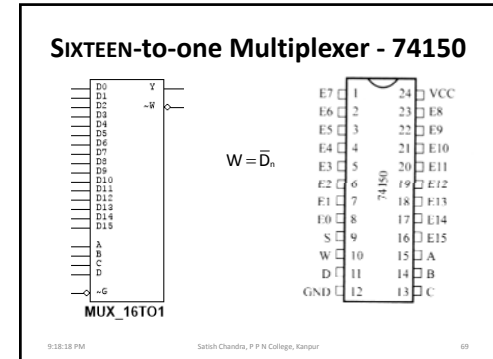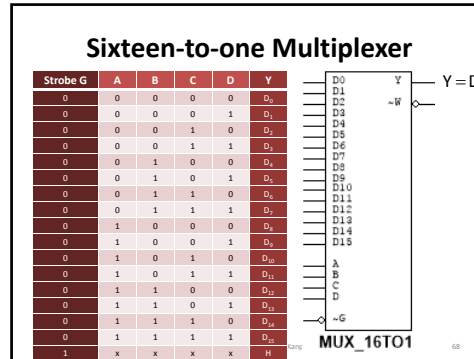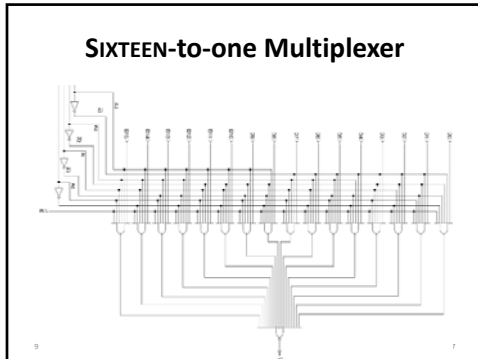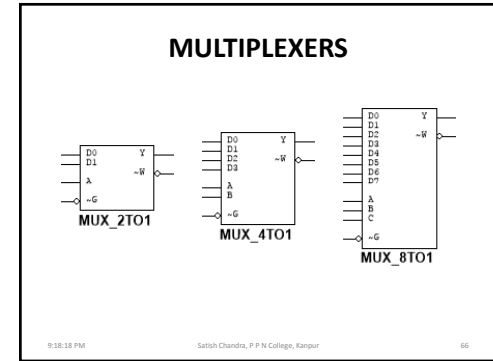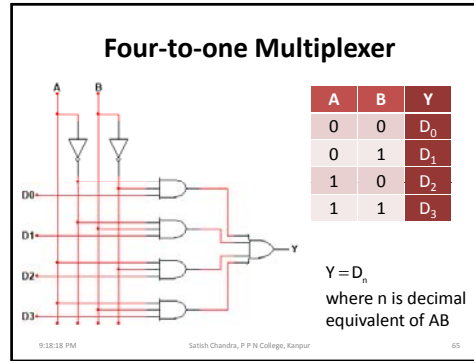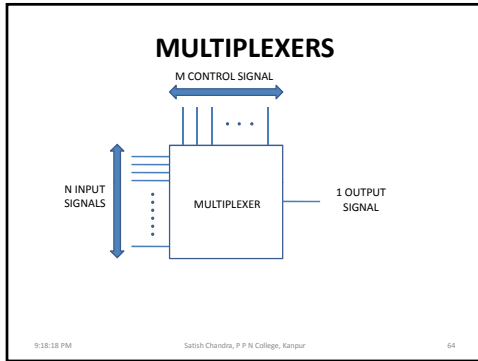
9:18:18 PM Satish Chandra, P P N College, Kanpur 63



DEMULTIPLEXERS

- Demultiplex means **one into many**.
- A circuit with only **one input** and **many outputs**.
- By applying **control signals**, input signal can be transmitted to any one of the output lines.

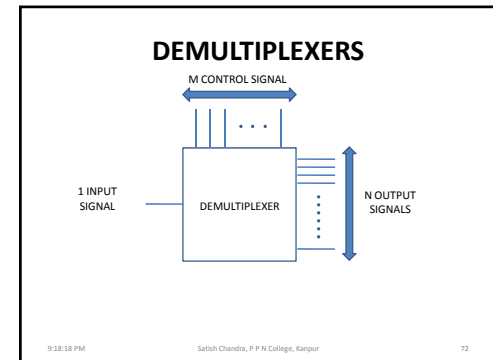9:18:18 PM Satish Chandra, P P N College, Kanpur 71



BCD TO DECIMAL DECODERS

- BCD stands for **Binary-Coded-Decimal**.
- A BCD number is a four-bit binary group that represents one of the ten decimal digits 0 through 9.
- Example: Decimal number 4926

Decimal	4	9	2	6
	↓	↓	↓	↓
BCD	0100	1001	0010	0110

9:18:18 PM Satish Chandra, P P N College, Kanpur 82

BCD TO DECIMAL DECODERS

9:18:18 PM Satish Chandra, P P N College, Kanpur 83

BCD TO DECIMAL DECODERS

No.	INPUTS				OUTPUTS										
	D	C	B	A	0	1	2	3	4	5	6	7	8	9	
0	L	L	L	L	H	H	H	H	H	H	H	H	H	H	H
1	L	L	L	H	L	H	L	H	L	H	L	H	L	H	L
2	L	L	H	L	H	L	H	L	H	L	H	L	H	L	H
3	L	L	H	H	L	H	L	H	L	H	L	H	L	H	L
4	L	H	L	L	H	L	H	L	H	L	H	L	H	L	H
5	L	H	L	H	L	H	L	H	L	H	L	H	L	H	L
6	L	H	H	L	H	L	H	L	H	L	H	L	H	L	H
7	L	H	H	H	L	H	L	H	L	H	L	H	L	H	L
8	H	L	L	L	L	H	L	H	L	H	L	H	L	H	L
9	H	L	L	H	L	H	L	H	L	H	L	H	L	H	L
INVALID	H	L	H	L	L	H	L	H	L	H	L	H	L	H	L
	H	L	H	H	L	H	L	H	L	H	L	H	L	H	L
	H	H	L	L	H	L	H	L	H	L	H	L	H	L	H
	H	H	L	H	L	H	L	H	L	H	L	H	L	H	L
	H	H	H	L	H	L	H	L	H	L	H	L	H	L	H
	H	H	H	H	L	H	L	H	L	H	L	H	L	H	L

9:18:18 PM Satish Chandra, P P N College, Kanpur 84

ENCODER

- An encoder converts non-digital data to digital data.
- An encoder has $n = 2^m$, input lines and m output lines.
- Only one of the input line will be active.
- The output lines generate a binary code corresponding to the that input line.

9:18:19 PM Satish Chandra, P P N College, Kanpur 85

ENCODER

9:18:19 PM Satish Chandra, P P N College, Kanpur 86

DECIMAL TO BCD ENCODER

9:18:19 PM Satish Chandra, P P N College, Kanpur 87

DECIMAL TO BCD ENCODER

- The decimal to BCD encoder with 10 inputs and 4 outputs. The switches 0 to 9 are push button switches like a pocket calculator.
- When button 3 is pressed, the C and D OR gates have high inputs, therefore output is ABCD=0011 i.e. decimal 3 is converted into its equivalent binary number 0011.
- Similarly, if you press button 5, the output will be ABCD=0101 and for switch 9, we get ABCD=1001

9:18:19 PM Satish Chandra, P P N College, Kanpur 88

DECIMAL TO BCD ENCODER - 74147

9:18:19 PM Satish Chandra, P P N College, Kanpur 89

DECIMAL TO BCD ENCODER - 74147

TRUTH TABLE

Inputs										Outputs			
X ₁	X ₂	X ₃	X ₄	X ₅	X ₆	X ₇	X ₈	X ₉	X ₀	A	B	C	D
H	H	H	H	H	H	H	H	H	H	H	H	H	H
X	X	X	X	X	X	X	X	X	L	L	L	L	L
X	X	X	X	X	X	X	L	H	L	L	L	L	L
X	X	X	X	X	L	H	H	H	L	L	L	L	L
X	X	X	X	L	H	H	H	H	L	L	L	L	L
X	X	X	L	H	H	H	H	H	L	L	L	L	L
X	X	L	H	H	H	H	H	H	L	L	L	L	L
L	H	H	H	H	H	H	H	H	H	H	H	H	L

9:18:19 PM Satish Chandra, P P N College, Kanpur 90