

Conversion of Galvanometer to Voltmeter

Object: To convert Weston galvanometer to a voltmeter of voltage range 0 to V volts.

Apparatus Used: battery, resistance box, galvanometer, voltmeter, rheostat, keys, connecting wires.

Formula Used: For the conversion of galvanometer to voltmeter (G→V) a high resistance 'R' is connected in series of galvanometer. The value of R is determined by following expression.

$$R = \frac{V}{I_g} - G$$

Here, V= maximum value of voltage range

G= galvanometer resistance

I_g =current for full scale deflection in galvanometer

$$I_g = C_s N$$

N= total number of divisions in galvanometer

C_s =Current sensitivity of galvanometer or figure of merit

$$C_s = \frac{E}{n(R' + G)}$$

E= e.m.f. battery or cell

R' = resistance involved in galvanometer circuit (in determination of determination C_s / I_g)

n= deflection (number of division) in galvanometer on introducing the resistance R' in galvanometer circuit.

Circuit Diagram:

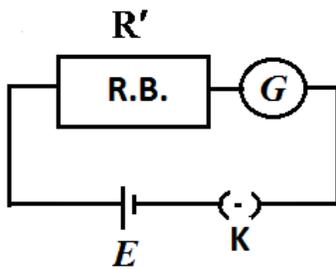


Figure (1)

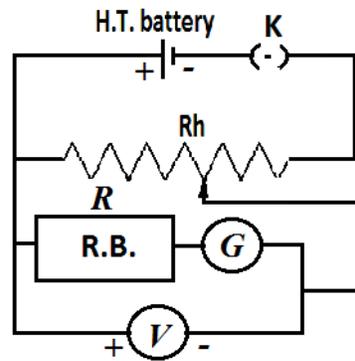


Figure (2)

Procedure:

1. Measure the e.m.f. of given cell/battery (E). Read the value of G written in galvanometer and total number of division (N) in galvanometer.
2. Make connections as shown in Figure (1).
3. Now close the key K . Note the value of deflection in galvanometer (n) with varying the resistance in resistance box (R').
4. Calculate the value of C_s for all set of R' and n using E and G. Now determine I_g with expression $I_g = C_s N$ and find the mean value of it.

- See in galvanometer, a value of current is written in it, this is I_g . If your calculated I_g is approximately same with this value then observation up to this point is correct. If it is not true then repeat/check the process 3→4.
- After it, calculate the value of R with the formula $R = \frac{V}{I_g} - G$. Now make the circuit shown in Figure 2 and introduce the calculated resistance R in resistance box.
- Now vary the deflection in galvanometer from 2→30 divisions in interval of 2 with help of rheostat and note the corresponding voltmeter readings (V).
- If V is maximum voltage of given voltage range then voltage equal to one division on galvanometer is V/N . Using it convert galvanometer deflections in volt (V').
- Now calculate the difference of V and V' . If value of V and V' are approximately same or their difference is too much small then the conversion of $G \rightarrow V$ is correct.

Observation:

- E=volt
- G= Ω
- N=
- Table for I_g

Sr.No.	$R'(\Omega)$	n	C_s	I_g (A)	mean I_g (in A or μ A)
1.	5000				
2.	6000				
3.	7000				
4.	8000				
5.	9000				
6.	10000				

5. Calibration of shunted galvanometer

Sr.No.	Galvanometer reading		Voltmeter reading V (in volt)	Error $V' - V$ (in volts)
	In division	In volt (V')		

Calculation: Show all calculations of C_s , I_g and R.

Result: The resistance required to convert the given galvanometer in to voltmeter of range of volts is(Ω).

Precaution:

Precautions:

- Resistance in determination of figure of merit should be of high value.
- Exact high resistance should be connected in series to galvanometer for conversion to voltmeter.
- Voltmeter should be connected using sign convention.
- Voltmeter used in calibration of shunted galvanometer should be of nearly same range.
- In calibration process the readings should be noted from zero.