

Power Amplifier

Satish Chandra
PPN PG College, Kanpur

Amplifier

- An amplifier is an electronic device used to increase the magnitude of voltage/current/power of an input signal.
- It takes in a weak electrical signal and reproduces a similar **stronger signal** at the output by using an external power source.

© Dr. Satish Chandra, Department of Physics, PPN PG College, Kanpur

Amplifier

- Depending on the changes it makes to the input signal, amplifiers are broadly classified into **Current, Voltage** and **Power amplifiers**.

© Dr. Satish Chandra, Department of Physics, J.N.P. College, Kanpur

Power Amplifier

- A **power amplifier** is an electronic amplifier designed to increase the magnitude of **power** of a given input signal.
- The power of the input signal is increased to a level high enough to **drive loads of output devices**.
- Like speakers, headphones, RF transmitters etc.


© Dr. Satish Chandra, Department of Physics, J.N.P. College, Kanpur

Power Amplifier

- A power amplifier is designed to drive loads directly and is used as a final block in an amplifier chain.
- The input signal to a power amplifier needs to be above a certain threshold. So, it is first pre-amplified using current/voltage amplifiers



Power Amplifier

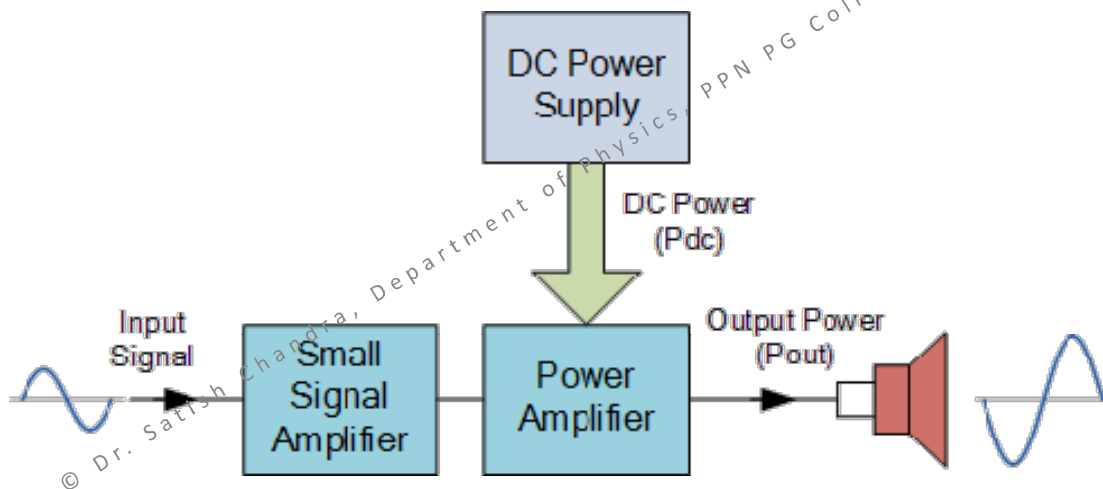

Power Amplifier Efficiency

- The efficiency of the amplifier in percentage,

$$\eta = \frac{P_{out}}{P_{dc}} \times 100$$

- P_{out} is the amplifier output power delivered to the load and P_{dc} is the DC power taken from the supply.
- It is very important that the amplifiers power supply is well designed to provide the **maximum** available continuous **power** to the **output** signal.


Types of Power Amplifiers

- Audio Power Amplifiers
- Radio Frequency Power Amplifiers
- DC Power Amplifiers

© Dr. Satish Chandra, Department of Physics, PPN PG College, Kanpur


Power Amplifier Classes

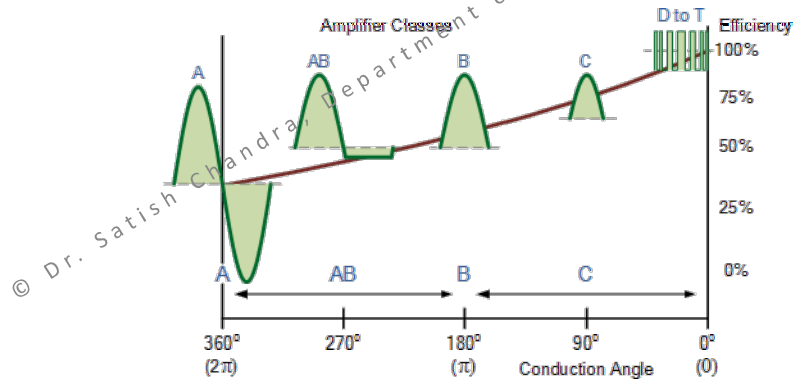- The most commonly used power amplifiers are the ones that are used in audio amplifier circuits and they come under classes A, B, AB or C.




Class A Power Amplifier

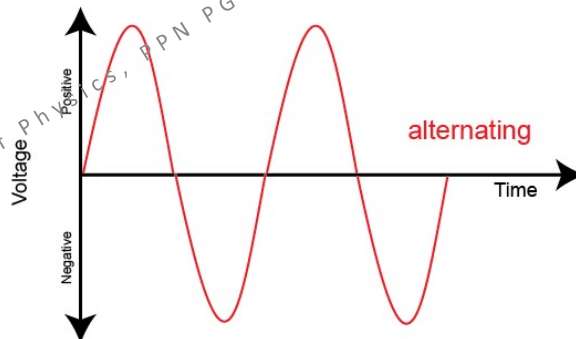- Analog waveforms are made up of positive and negative halves of the waveform.
- In **class A amplifiers**, the entire input waveform is used in the amplification process.



Class A Power Amplifier

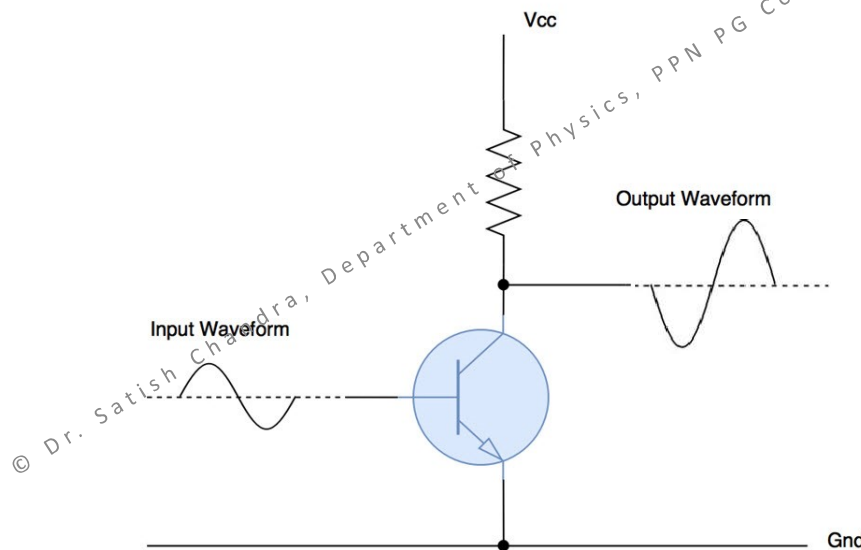

Class A Power Amplifier

- The Class A amplifier is the simplest form of power amplifier that uses a **single switching transistor** in the standard **common emitter** circuit configuration to produce an **inverted output**.
- The transistor is always **biased "ON"** so that it conducts during one complete cycle of the input signal waveform producing **minimum distortion** and **maximum amplitude** of the output signal.


Class A Amplifiers

- This single output transistor is biased around the Q-point within the middle of its load line and so is never driven into its cut-off or saturation regions thus allowing it to conduct current over the full 360 degrees of the input cycle.
- Then the output transistor of a class-A never turns "OFF" which is one of its main disadvantages.

Class A Power Amplifier

- Class A power amplifier output stages may use a **single power transistor** or **pairs of transistors** connected together to share the high load current.

Single Stage Class A Amplifier Circuit

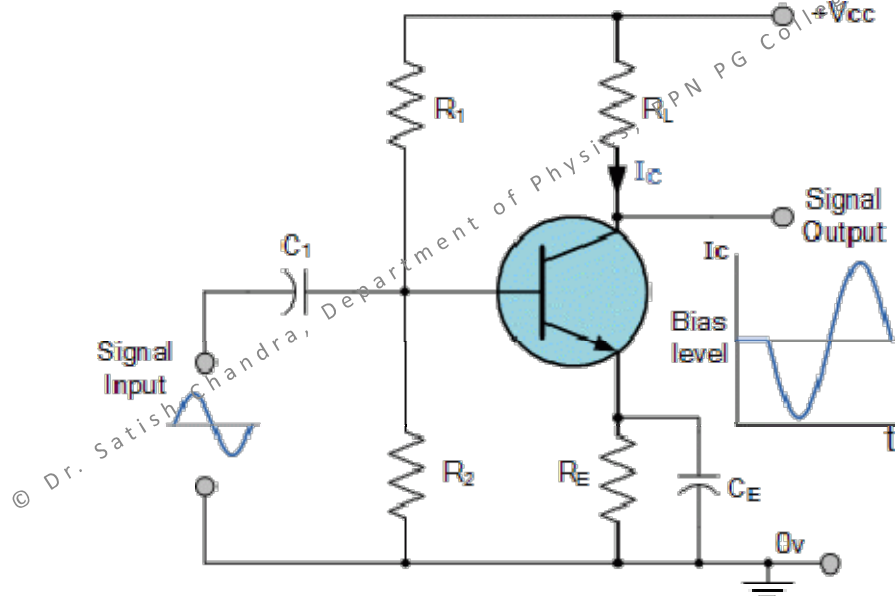

Single Stage Class A Amplifier Circuit

- This is the simplest type of Class A power amplifier circuit.
- It uses a single-ended transistor for its output stage with the resistive load connected directly to the Collector terminal.
- When the transistor switches "ON" it sinks the output current through the Collector resulting in a voltage drop across the Emitter resistance .


Single Stage Class A Amplifier Circuit

- Throughout the input signal, the transistor remains in forward bias mode.
- In this class, the transistor remains in active mode all the time even if there is no input signal, which leads to excessive heat generation thus causing a reduction in the efficiency.
- The efficiency of class A amplifiers is **25% in normal configuration** and **50% in a transformer coupled configuration**.

Single Stage Class A Amplifier Circuit


- When the input voltage is applied at the base terminal of the transistor operating in CE mode it leads to variation in base current, this variation in I_B produces similar variation in collector current I_C and the output is taken across the load.
- The applied input signal fluctuates the **collector current from max to min** which resultantly moves the Q point along the load line.

Load Line & Q Point

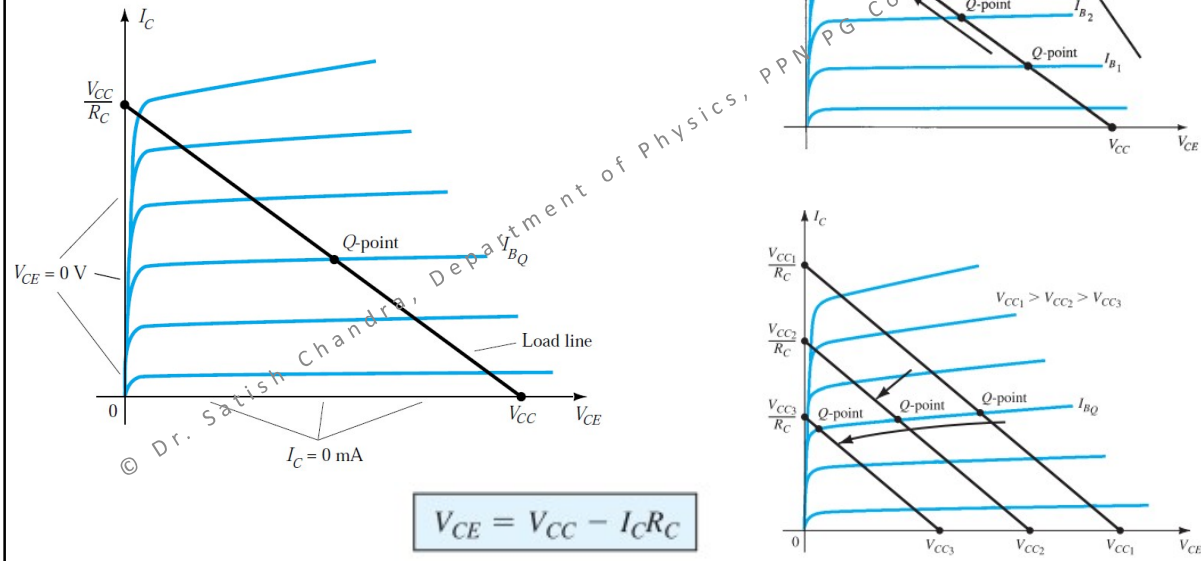


Class A Amplifier Circuit

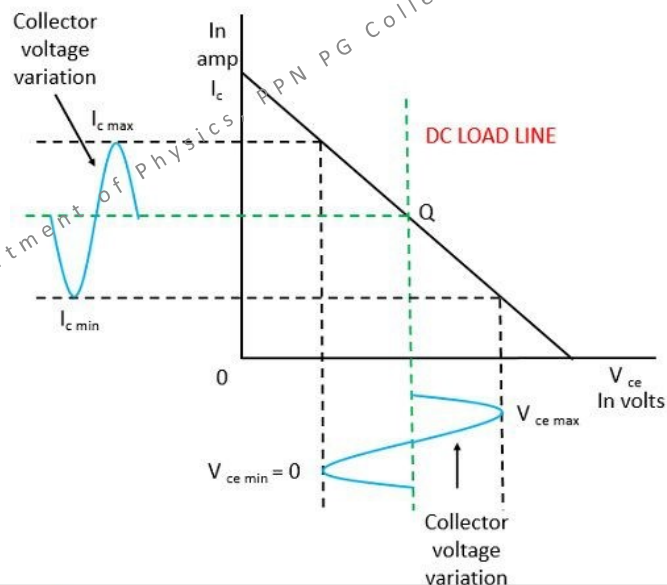- It operates in the linear portion of its characteristic curves, the single output device conducts through a full 360 degrees of the output waveform.




Class A Amplifier Circuit

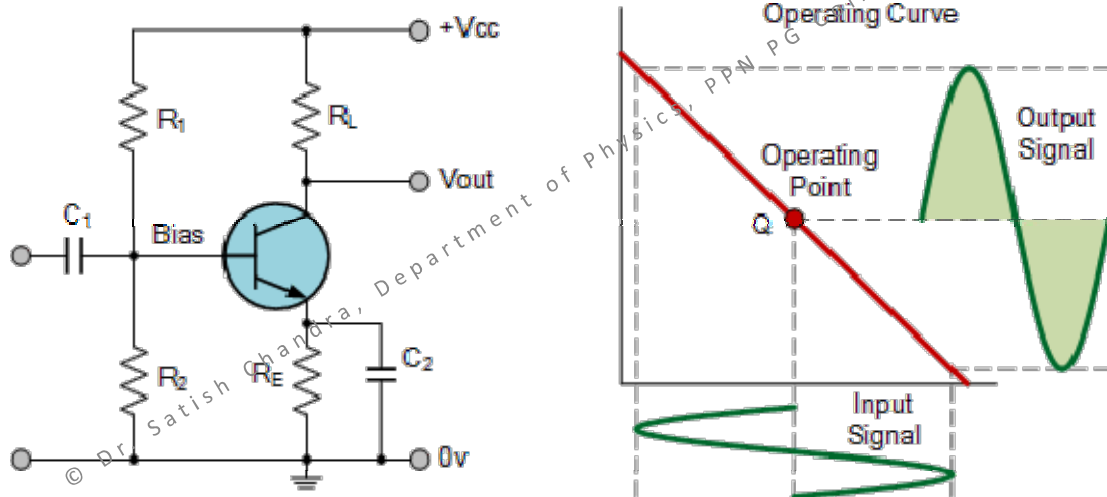

Darlington Transistor Configurations

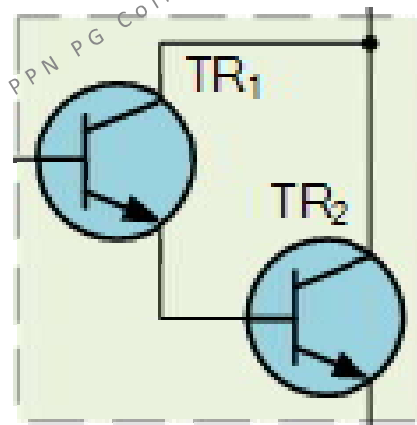
- Another simple way to increase the **current handling capacity** of the circuit while at the same time obtain a **greater power gain** is to replace the single output transistor with a **Darlington Transistor Pair**.



Darlington Transistor Configurations

- These types of devices are basically two transistors within a single package, one small **pilot transistor** and another larger **switching transistor**.
- The big advantage of these devices are that the **input impedance is suitably large** while the **output impedance is relatively low**, thereby **reducing the power loss** and therefore the **heat** within the switching device.

Darlington Transistor Configurations

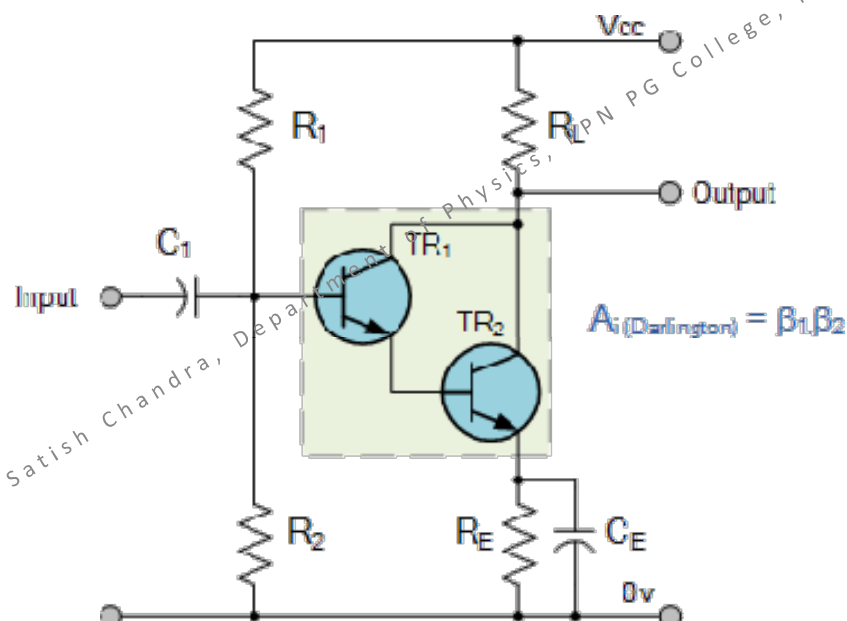

Darlington Transistor Configurations

- The overall current gain β of a Darlington Pair is the product of the two individual gains of the transistors multiplied together.
- A very high β values along with high Collector currents are possible compared to a single transistor circuit.


© Dr. Satish Chandra, Department of Physics, J. N. P. College, Kanoor

Transformer-coupled Amplifier Circuit

- A transformer connected directly in the Collector circuit to form a circuit called a **Transformer Coupled Amplifier**.
- The transformer **improves the efficiency** of the amplifier by matching the impedance of the load with that of the amplifiers output using the turns ratio (N_s/N_p) of the.

© Dr. Satish Chandra, Department of Physics, J. N. P. College, Kanoor

Transformer-coupled Amplifier Circuit

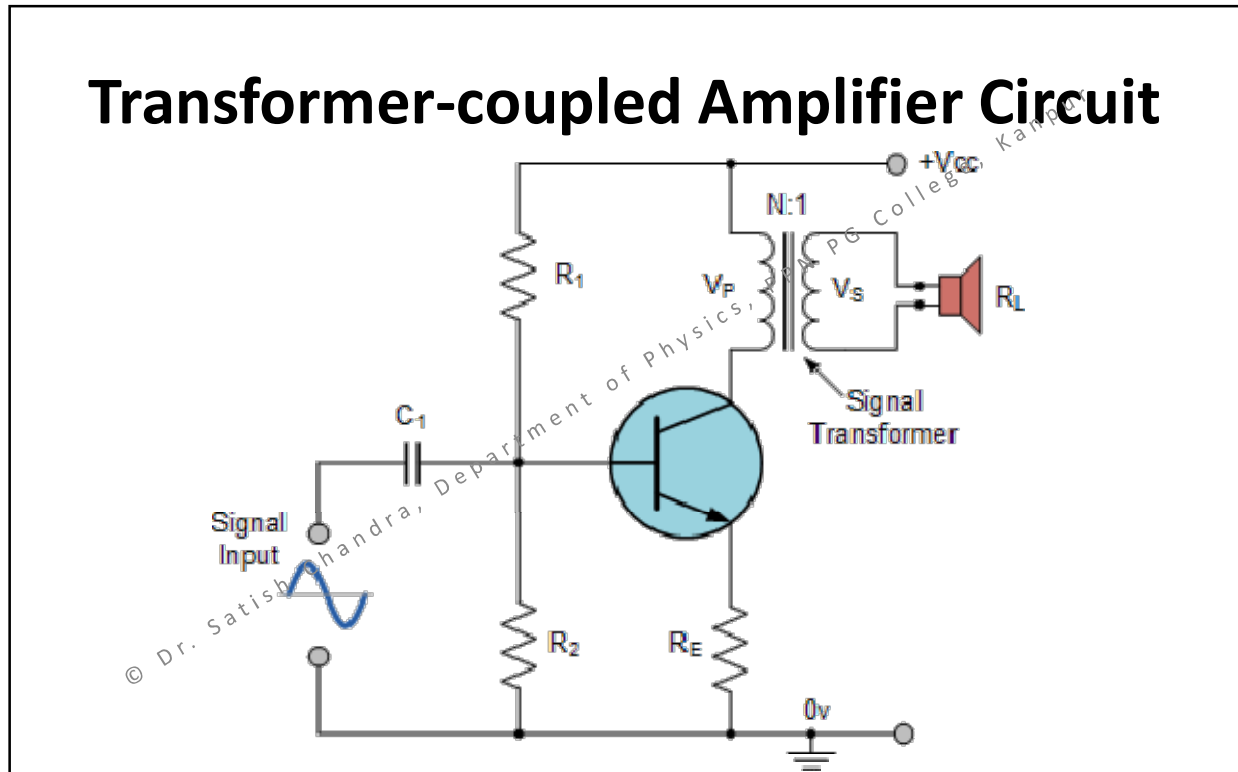

Transformer-coupled Amplifier Circuit

- As the Collector current, I_C is reduced to below the quiescent Q-point set up by the base bias voltage, due to variations in the base current, the magnetic flux in the transformer core collapses causing an induced *emf* in the transformer primary windings.
- This causes an instantaneous collector voltage to rise to a value of **twice the supply voltage $2V_{CC}$** giving a maximum **collector current of twice I_C** when the Collector voltage is at its minimum.

Class A Power Amplifier

- **Advantages:**
 - It provides distortionless amplification.
 - Small signal can be amplified.

© Dr. Satish Chandra, Department of Physics, PPN PG College, Kanpur

Class A Power Amplifier

- **Disadvantages:**
 - Collector efficiency is low.
 - Output power is low.
 - Due to excessive heat generation, heat sinks are needed which makes them costly and bulky.

© Dr. Satish Chandra, Department of Physics, PPN PG College, Kanpur

Class B Power Amplifier

- Class B power amplifiers are designed to **reduce the efficiency and heating problems** present in the class A amplifiers.
- Instead of a single transistor to amplify the entire waveform, this class of amplifiers use **two complementary transistors**.


© Dr. Satish Chandra, Department of Physics, P.N.P. College, Kanpur

Class B Power Amplifier

- One transistor amplifies positive half of the waveform and the other amplifies negative half of the waveform.
- So each active device conducts for one half (180°) of the waveform and two of them when combined amplify the entire signal.

© Dr. Satish Chandra, Department of Physics, P.N.P. College, Kanpur

Class B Power Amplifier

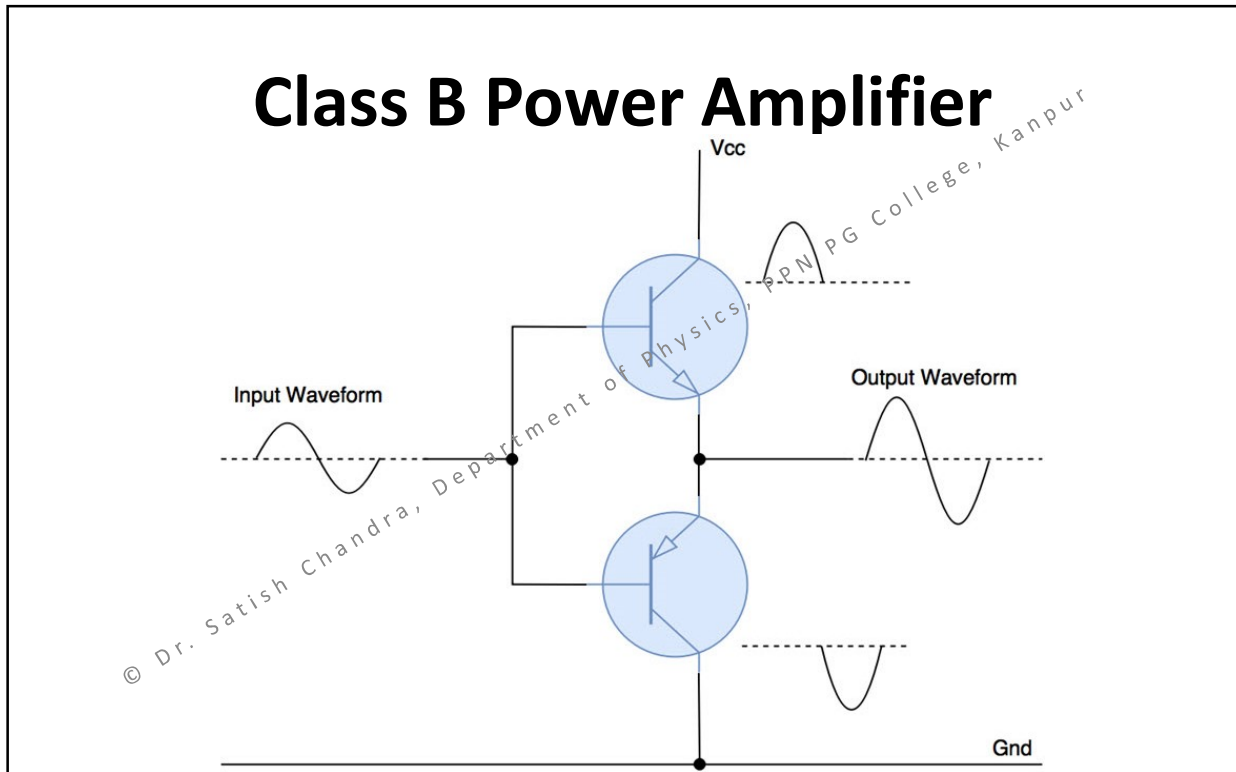


Class B Power Amplifier

- When the input signal goes positive, the positive biased transistor conducts while the negative transistor is switched “OFF”
- Likewise, when the input signal goes negative, the positive transistor switches “OFF” while the negative biased transistor turns “ON” and conducts the negative portion of the signal.
- The transistor conducts only half of the time, either on positive or negative half cycle of the input signal.

Class B Power Amplifier

- A Class B Amplifier is also known as a **push-pull amplifier**.
- Push-pull amplifiers use two “complementary” or matching transistors, one being an **NPN-type** and the other being a **PNP-type**.
- Both power transistors receive the same input signal together that is equal in magnitude, but in opposite phase to each other.

Class B Push Pull Amplifier

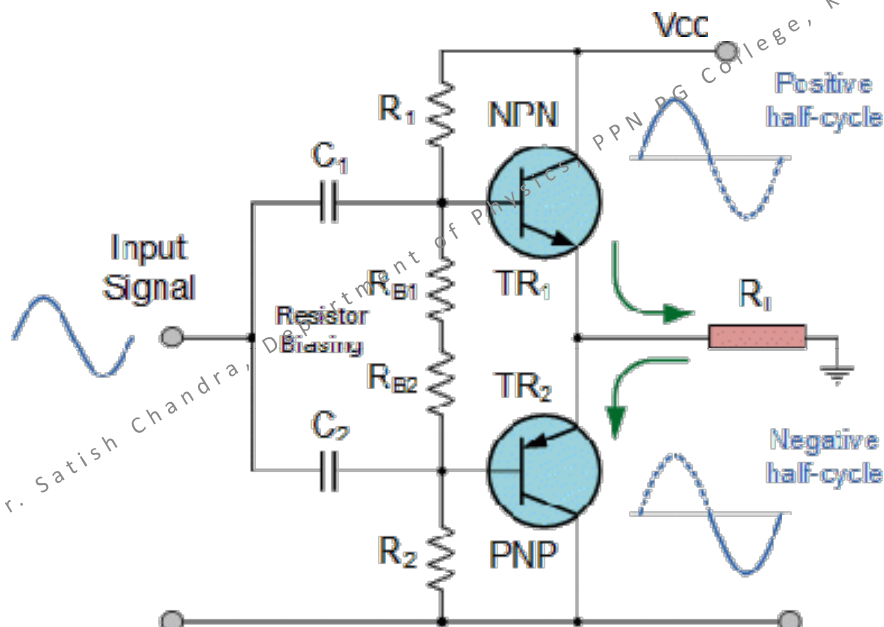

Class B Power Amplifier

- Then the conduction angle for this type of amplifier circuit is only 180° or 50% of the input signal.
- This pushing and pulling effect of the alternating half cycles by the transistors gives this type of circuit its “push-pull” name.
- But are more generally known as the **Class B Amplifier**

Class B Power Amplifier


- A **Class B** standard circuit that uses a balanced **center-tapped input transformer**, which splits the incoming waveform signal into two equal halves and which are 180° out of phase with each other.
- Another **center-tapped transformer** on the **output** is used to recombined the two signals providing the increased power to the load.

Class B Power Amplifier

- The transistors used for this type of **transformer push-pull amplifier** circuit are **both NPN transistors** with their emitter terminals connected together.

© Dr. Satish Chandra, Department of Physics, JPN PG College, Kanpur


Class B Power Amplifier

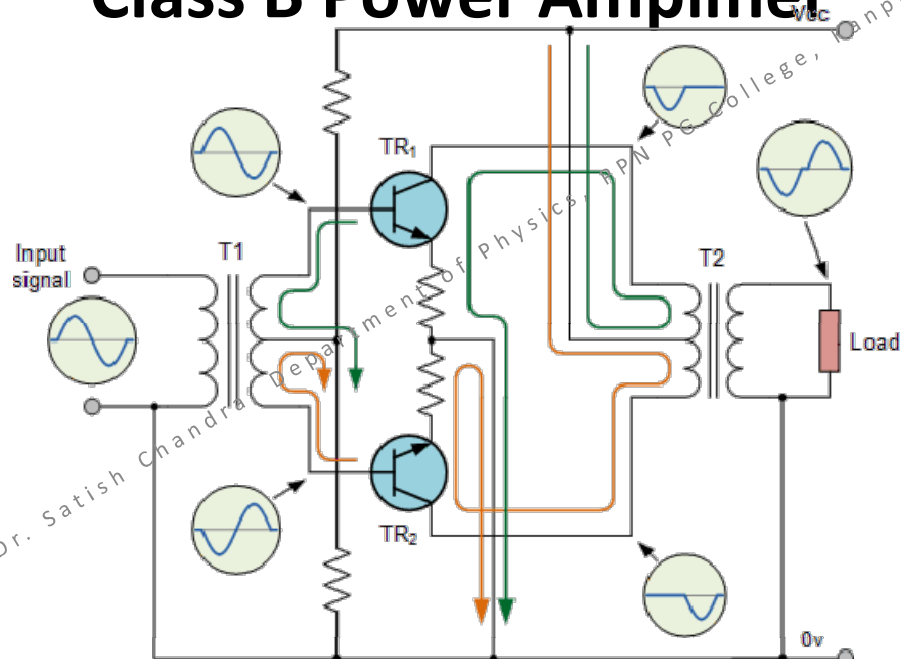

Class B Power Amplifier

- **Class B Amplifier** operation has **zero DC bias** as the transistors are biased at the **cut-off**, so each transistor only conducts when the input signal is greater than the Base-emitter voltage.
- Therefore, **at zero input there is zero output** and no power is being consumed.
- This then means that the actual Q-point of a Class B amplifier is on the V_{CE} axis of the load line.

Class B Power Amplifier

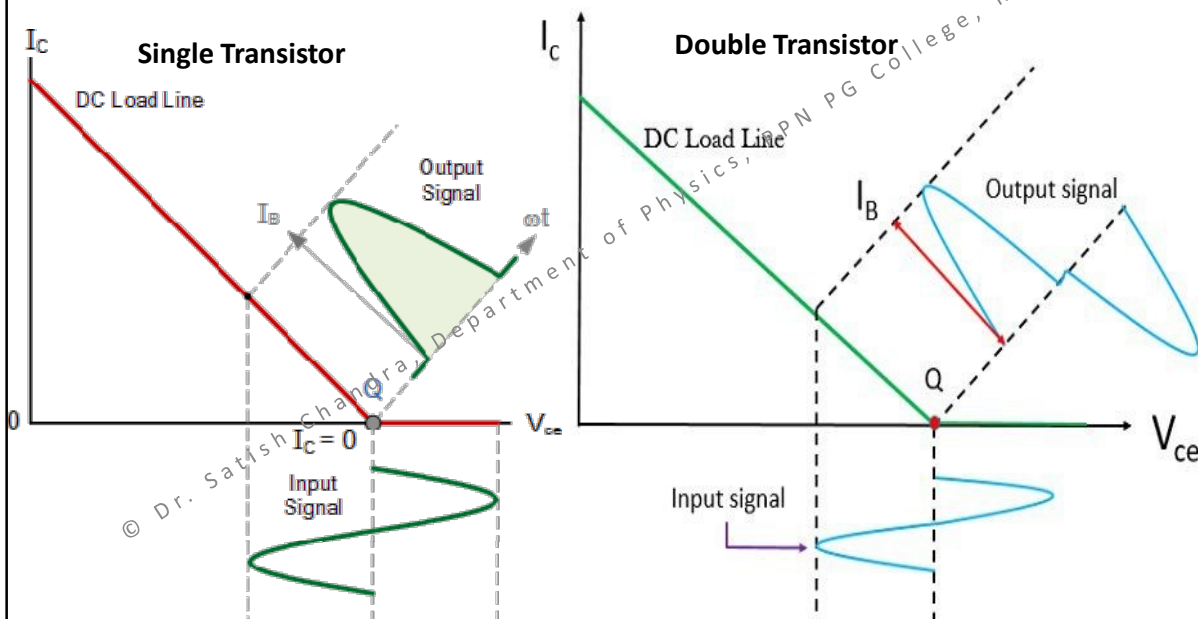


Class B Power Amplifier

- The **Class B Amplifier** has the big advantage over their Class A amplifier in that **no current flows through the transistors with no input signal**.
- Therefore, **no power is dissipated** in the output transistors or transformer when there is no signal present unlike Class A amplifier stages, that require significant base bias thereby dissipating lots of heat – even with no input signal present.

Class B Power Amplifier

- So the overall **conversion efficiency** (η) of the amplifier is greater than Class A amplifier with efficiencies reaching **as high as 70%**.
- But, because of superposition of two halves of the waveform, there exists a small distortion at the crossover region.

Crossover Distortion

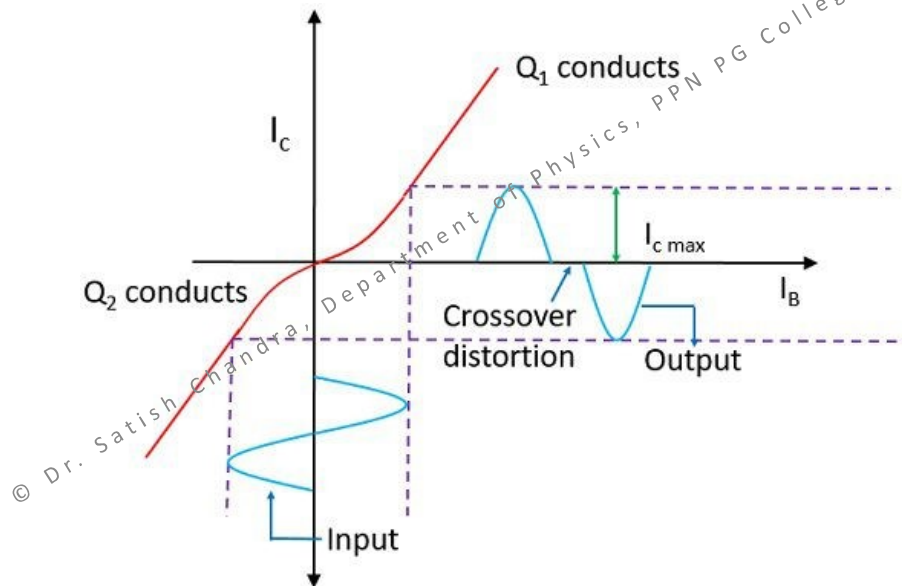

Class B Power Amplifier

- Working of class B leads to **crossover distortion** because as we know the voltage of 0.7 Volt is required by the transistor to start its conduction so transistor will not be active below 0.7 Volt.
- This means that the portion of the wave will not get reproduced at the output leading to distorted output.
- This zero crossing distortion is called **crossover distortion**.


Class B Power Amplifier

- **Advantages:**
 - It is more efficient as compared to the class A power amplifier.
 - Even harmonics are avoided because of the push-pull mechanism.
- **Disadvantages:**
 - It leads to crossover distortion.
 - The cost and size are increased because of coupling transformers.

Class AB Amplifier

- A simple way to eliminate crossover distortion in a Class B amplifier is to add two small voltage sources to the circuit to bias both the transistors at a point slightly above their cut-off point.
- This then would give us what is commonly called an **Class AB Amplifier** circuit.
- However, it is impractical to add additional voltage sources to the amplifier circuit so PN-junctions are used to provide the additional bias in the form of silicon diodes.

Class AB Amplifier

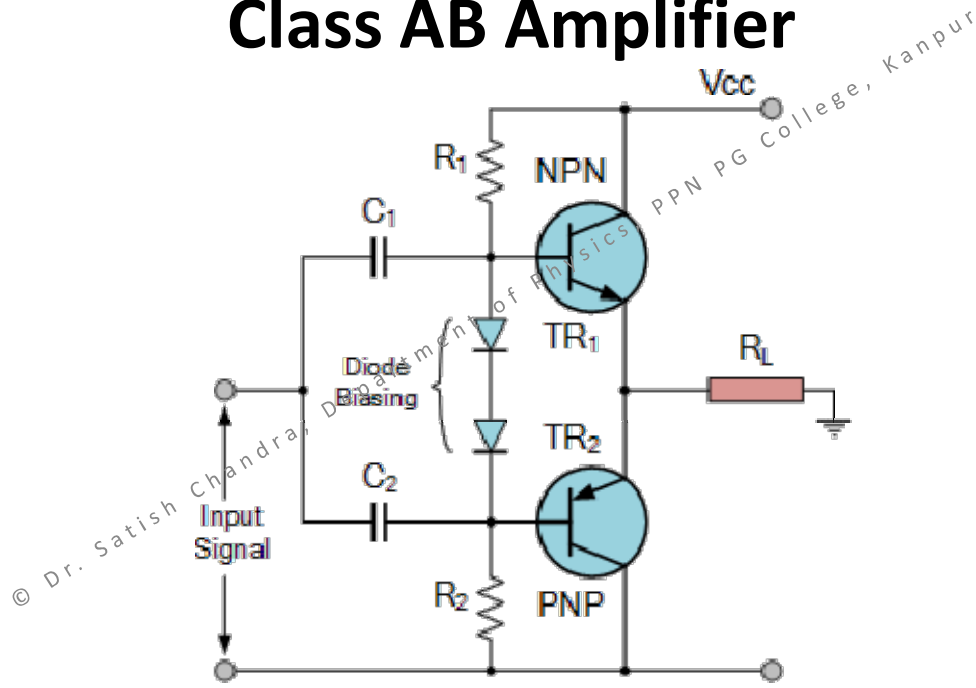


Class AB Amplifier

- A small constant current flows through the series circuit of R_1 - D_1 - D_2 - R_2 , producing voltage drops which are symmetrical either side of the input. With no input signal voltage applied, the point between the two diodes is zero volts.
 - As current flows through the chain, there is a forward bias voltage drop of approx. 0.7V across the diodes which is applied to the base-emitter junctions of the switching transistors.
- © Dr. Satish Chandrar Department of Physics PPN PG College, Kanpur


Class AB Amplifier

- Therefore the voltage drop across the diodes, biases the base of transistor TR1 to about 0.7 volts, and the base of transistor TR2 to about -0.7 volts.
- Thus the two silicon diodes provide a constant voltage drop of approximately 1.4 volts between the two bases biasing them above cut-off.

Class AB Amplifier

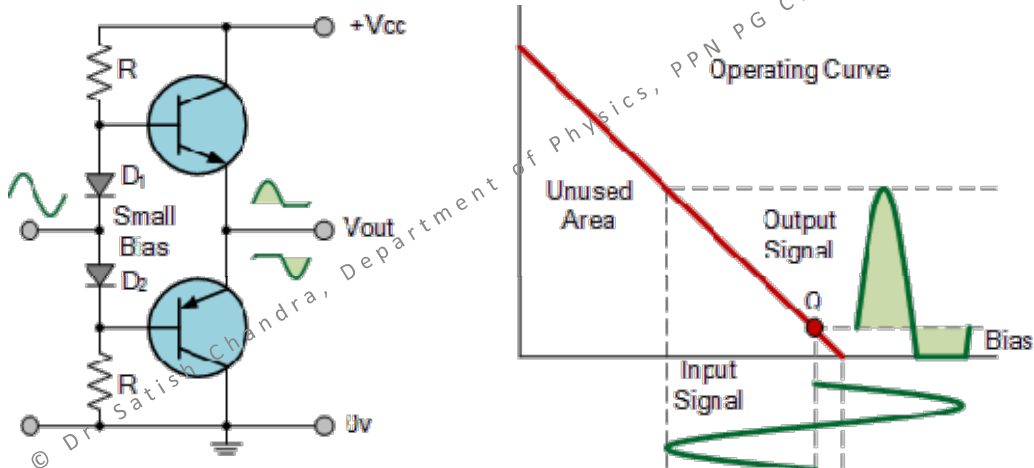

Class AB Amplifier

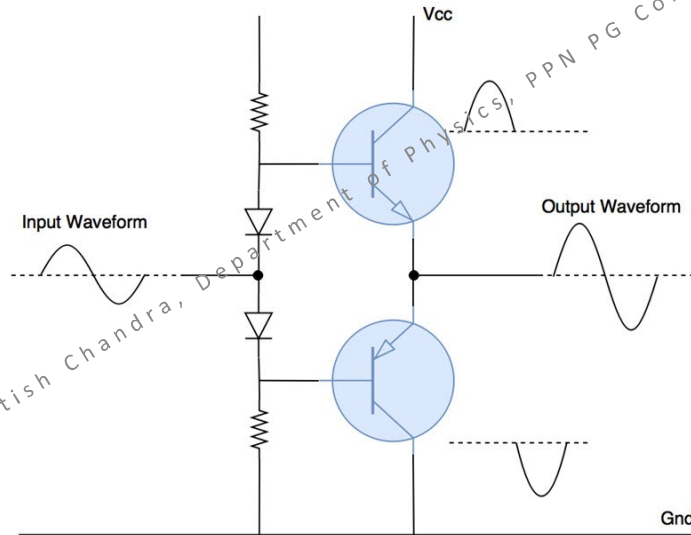


Class AB Amplifier

- The advantage of this small bias voltage, provided by series diodes or resistors, is that the crossover distortion created by the class B amplifier characteristics is overcome, without the inefficiencies of the class A amplifier design.
- So the class AB amplifier is a good compromise between class A and class B in terms of efficiency and linearity, with conversion efficiencies reaching about 50% to 60%.

Comparison of the Different Amplifier Classes

- **Class A:** – The amplifiers single output transistor conducts for the full 360° of the cycle of the input waveform.
- **Class B:** – The amplifiers two output transistors only conduct for one-half, that is, 180° of the input waveform.
- **Class AB:** – The amplifiers two output transistors conduct somewhere between 180° and 360° of the input waveform.

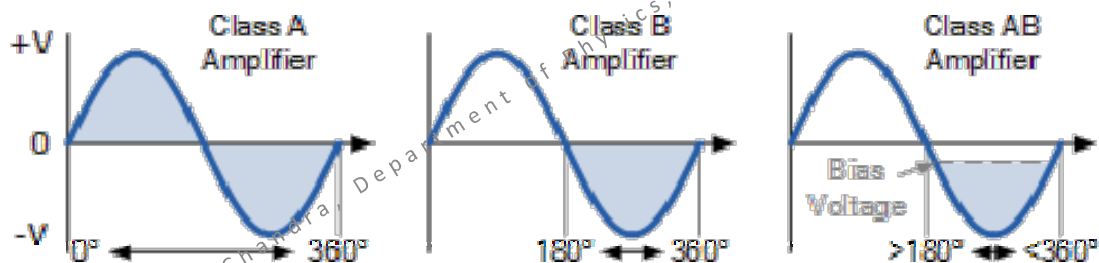Comparison of the Different Amplifier Classes




Distortion

- Distortion can be defined as the **changes that occur in output from input** during operation.
- It is always suggested to have a **distortionless** output.
- Distortion in Amplifier basically implies the **variation in the waveform received at the output** with respect to the applied input.
- The **unwanted alterations** generated during amplification is known as **distortion**.

Distortion

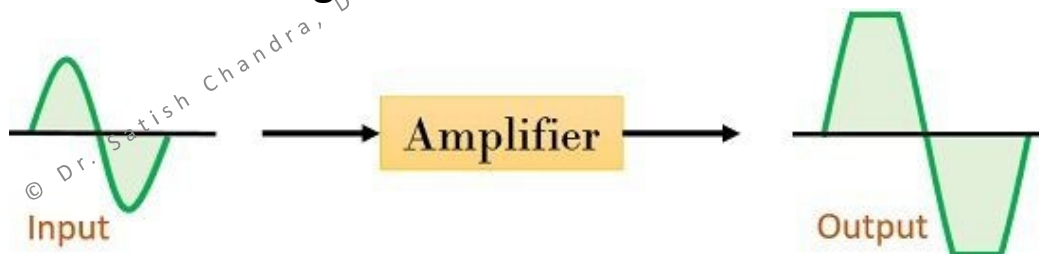
- A pure signal always has a single frequency component where voltage varies positive and negative by an equal amount.
- If this variation is less than full 360° cycle, then it is said that the signal is distorted.



Reasons for signal distortion

- Due to **incorrect biasing** when the signal is not amplified for the entire cycle of the input signal then distortion occurs.
- It also occurs in the case when the applied **input signal is very large**.
- Distortion in amplifier sometimes results when the **amplification is not linear** over the complete frequency range.

Types of Distortion in Amplifier

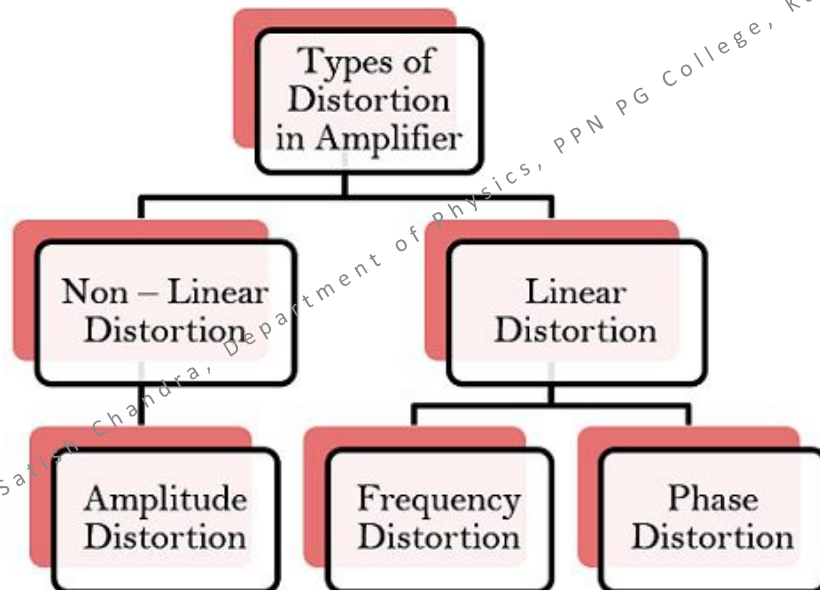


Amplitude Distortion

- Distortion occurs due to **attenuation in the peak value** of the waveform.
- The shift in “Q point” and amplification for less than 360° of the input signal leads to amplitude distortion.
- It occurs mainly due to **incorrect biasing and clipping**.


Amplitude Distortion

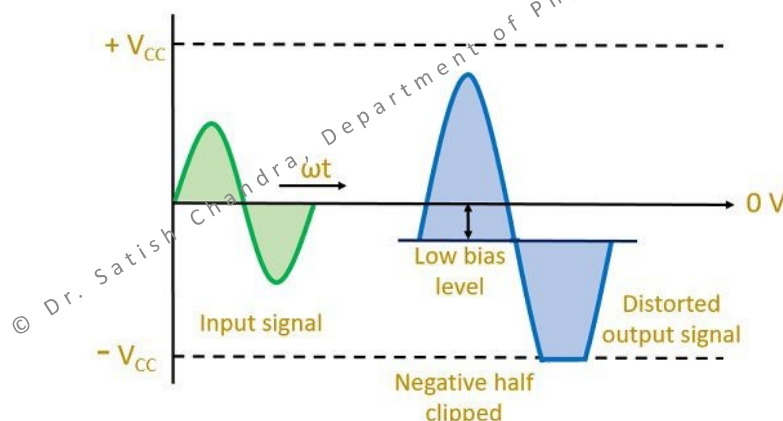- Suppose insufficient biasing is provided, the Q point will lie near the lower half of the load line. In such condition, **negative half** of input is **clipped**




Amplitude Distortion

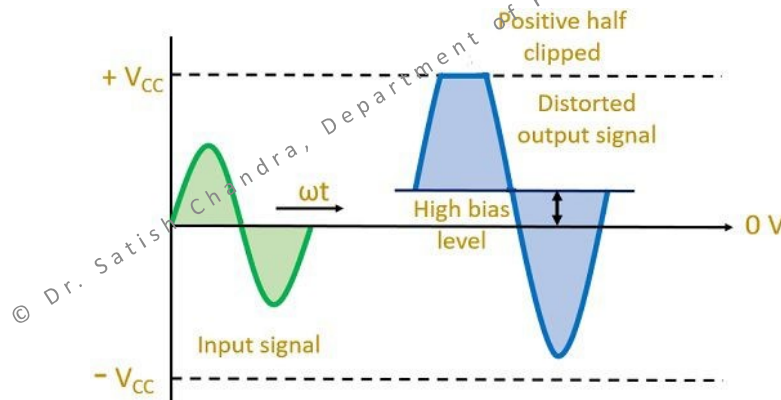- Suppose an extra bias potential is provided, the “Q point” will now be at the upper half of the load line. This condition gives an output that is **cut-off at positive half** of the waveform.




Amplitude Distortion

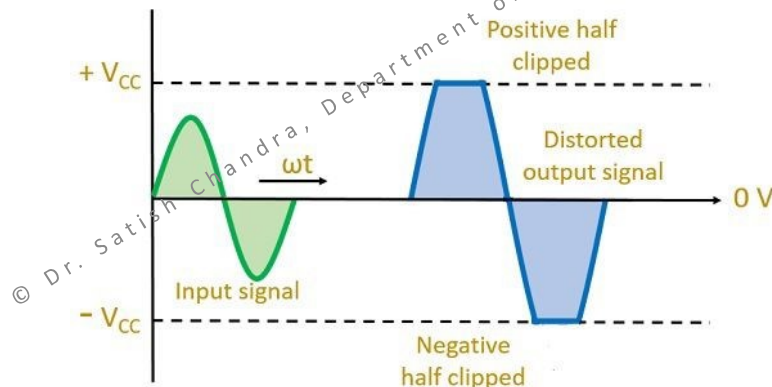- When large input signal is amplified by the gain of the amplifier, both **positive and negative half** of the waveform gets **clipped**. This is also known as **clipping distortion**.




Frequency Distortion

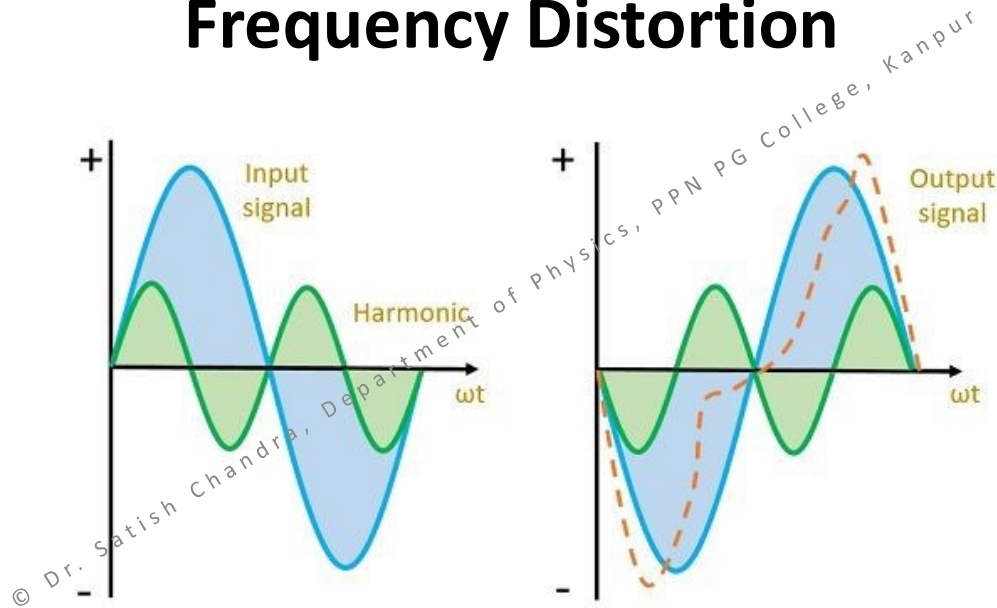

Frequency Distortion

- The input consists of fundamental frequency along with harmonics.
- The combination of the two on amplification will give a distorted signal at the output.
- It occurs either due to the presence of reactive elements or by the electrode capacitances of the amplifier circuits.

Phase Distortion

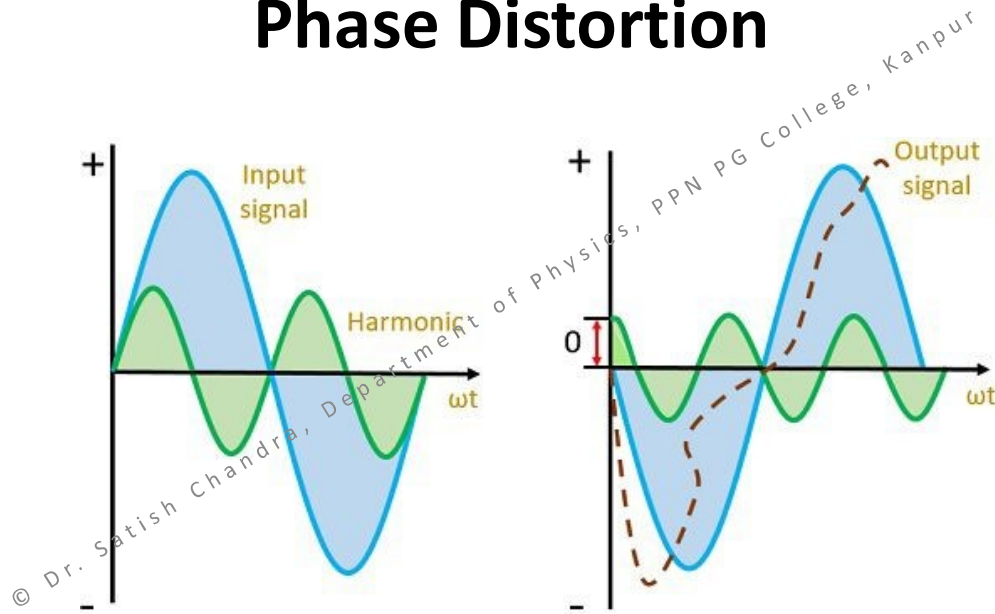

Phase Distortion

- Phase Distortion in the amplifier is also known as **delay distortion**.
- Whenever there is a time delay between input and occurrence of the signal at the output. It is said to be phase distorted signal.
- It occurs mainly due to electrical reactance.
- A signal consists of different frequency components. So, when different frequency suffers different phase shift, phase distortion takes place.