

LCR-Circuits

Object: To determine the impedance of LCR circuit.

Apparatus Used: resistance, inductor coil, capacitor, connecting wires, a.c. voltmeter, milli-ammeter, low voltage a.c. source.

Formula Used: The following formula is used for the determination of impedance of LCR circuit.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Where, Z : impedance of LCR circuit,

R : resistance

X_L : Inductive reactance,


X_C : Capacitive reactance

$$R = \frac{dV_R}{dI_R}, \quad X_L = \frac{dV_L}{dI_L} \quad \text{and} \quad X_C = \frac{dV_C}{dI_C}$$

V_R , V_L and V_C are the voltage across R, L and C respectively.

I_R , I_L and I_C are the currents through R, L and C respectively.

Circuit Diagram:

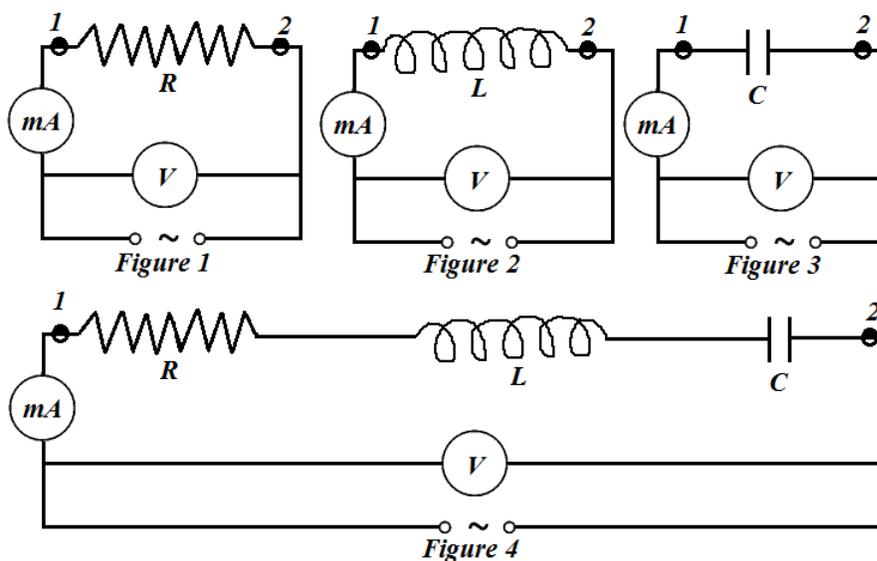

Procedure:

1. Note: In the given apparatus the a.c. source, voltmeter and milli-ammeter are internally connected. The two points 1 and 2 are given for rest connections. So connect resistor or inductor or capacitor or series of all with points 1 and 2 to complete the circuit.
2. Initially make the circuit as shown in Figure 1. Now vary the voltage across R with help of given knob in apparatus, and note the corresponding current. This will provide you the values of V_R and I_R . Plot the graph in V_R and I_R . the slope of this graph will give the value of R.
3. Now make the circuit as shown in Figure 2. Now vary the voltage across L with help of given knob in apparatus, and note the corresponding current. This will provide you the values of V_L and I_L . Plot the graph in V_L and I_L . The slope of this graph will give the value of X_L .

- Similarly, make the circuit as shown in Figure 3. Now vary the voltage across C with help of given knob in apparatus, and note the corresponding current. This will provide you the values of V_C and I_C . Plot the graph in V_C and I_C . The slope of this graph will give the value of X_C .
- After it, make the circuit as shown in Figure 4. Now vary the voltage across combination of R, L and C with help of given knob in apparatus, and note the corresponding current. This will provide you the values of V and I. Plot the graph in V and I. The slope of this graph will give the value of Z.
- Further more calculate the value of z with the help of R, X_L and X_C . This value should be equal or approximately equal to the value of z obtained with graph.

Observation:

- Least count of voltmeter= volts
- Least count of mili-ammeter= mA
- Table for value of voltage and current

Sr.No.	R-Circuit		L-Circuit		C-Circuit		LCR-Circuit	
	V_R (volt)	I_R (mA)	V_L (volt)	I_L (mA)	V_C (volt)	I_C (mA)	V (volt)	I (mA)
1.								
2.								
3.								
4.								
5.								
6.								

Calculation:

- Show the evaluation of R, X_L , X_C and Z with graph.
- Show the calculation of Z with the evaluated values of R, X_L , and X_C .

Result:

- R= Ω
- X_L = Ω
- X_C = Ω
- Z_{graph} = Ω
- $Z_{calculated}$ = Ω

Precaution:

- Connections should be tight.
- Variation in voltage should be in slow manner.
- Reading of voltage and current should be started with zero.